 


# VLSI PROJECT- ALU

Goal : Design an ALU that can perform a 4-Bit addition, subtraction, comparison, ANDing.


Design:



Decoder:


S1	S0	Operation
0	0	Add
0	1	Subtract
1	0	Comparator
1	1	And

 Constructed using a 2:4 decoder: Two selection lines S0 and S1 given as input to decide the operation






Enable blocks:

 For every operation, the inputs A and B are sent to the enable block where they are individually ANDed with the their respective decoder output.



4 Bit Full Adder:

Made using four 1-bit full adders:

 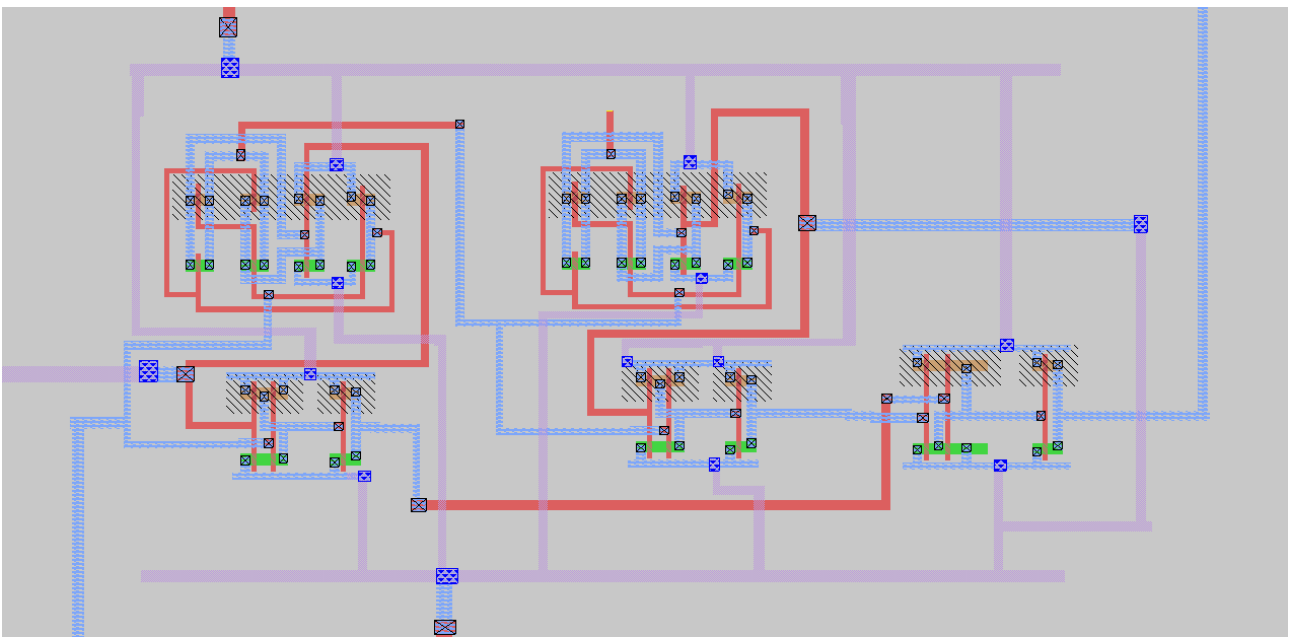 


Output was 5 bit to take account of the final carry bit.

## 4 Bit Full subtractor


The Input B was first XORed with D1 and a carry of 1 was given to the first full adder to take two's complement and add it to input A. As a result the outputs are in 2's complement.


### XOR block

 


### Comparator:

Logic used:

 


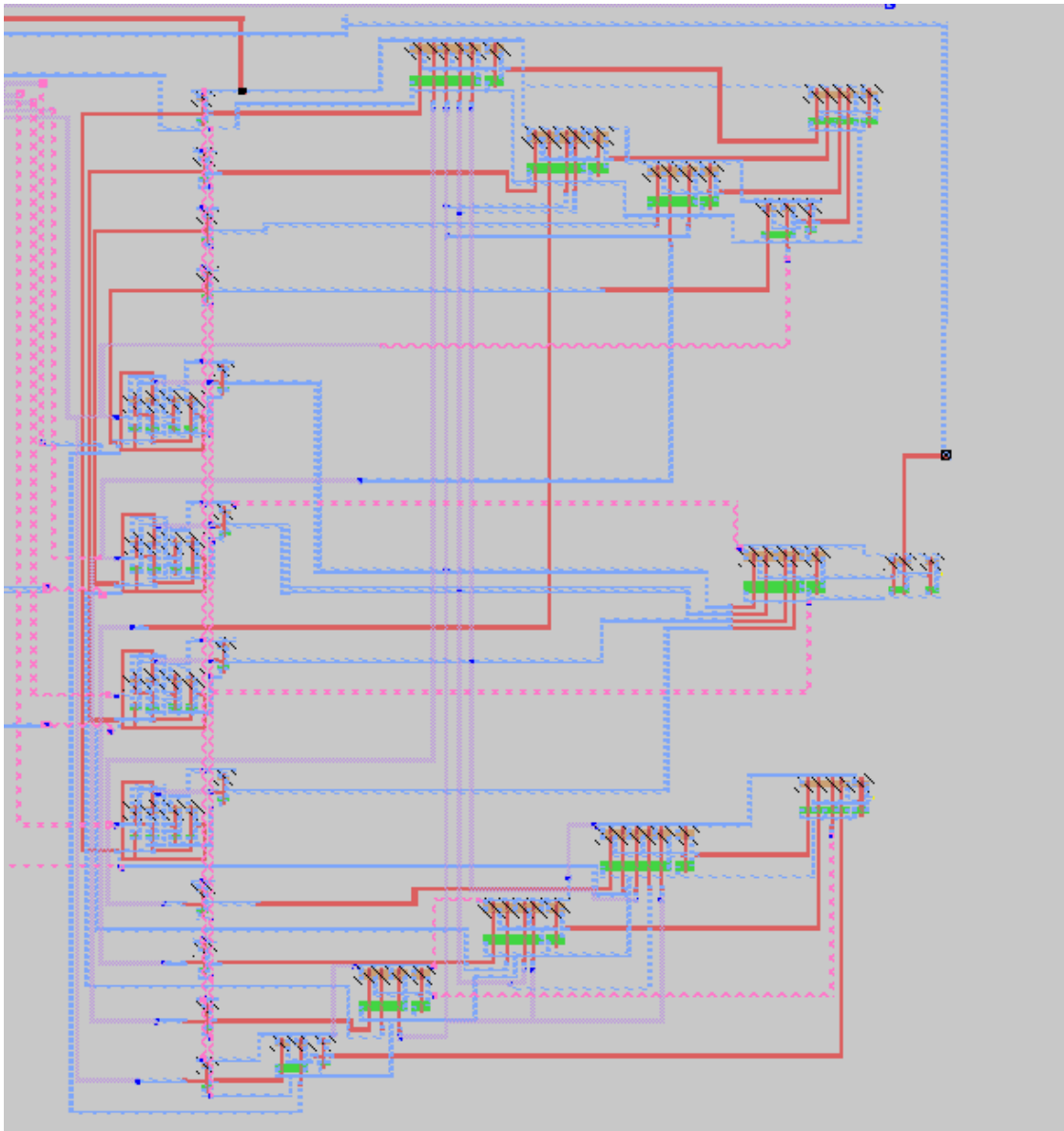

 
AND block:  
Finally D3 and the inputs A and B




INPUTS:  
Selection lines

 


Input A

 


Input B

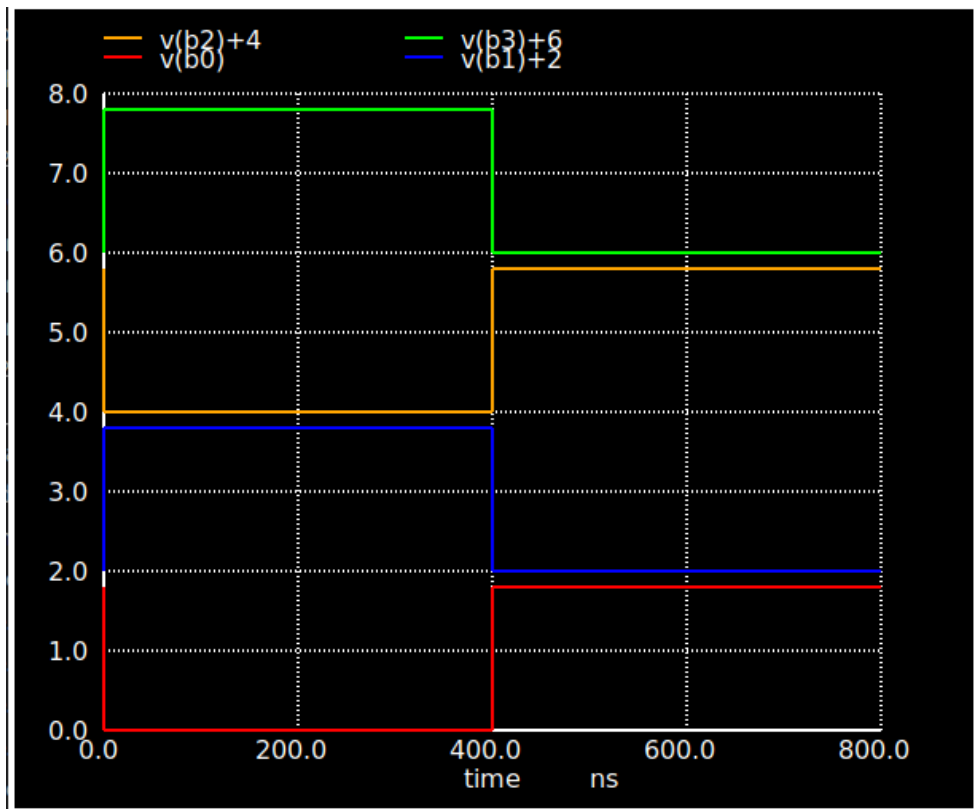

OUTPUTS:  
Decoder

 


Full adder:

 


Full Subtractor:




 

Comparator:

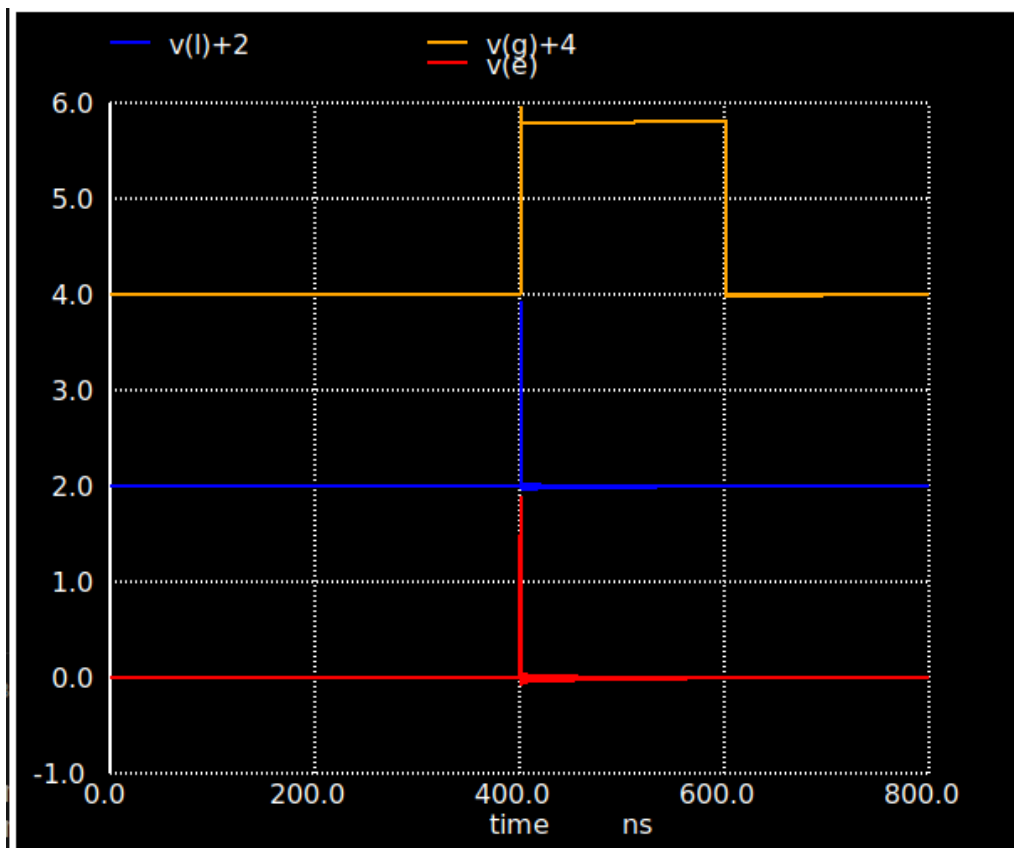


And Block:

 

## DELAY ANALYSIS:

Critical path : Path with maximum delay

Adder

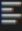Delay_Analysis >  output_add.txt			
1	5.50721e-10	input = a0	output = sum0
2	5.14249e-10	input = a0	output = sum1
3	4.79123e-10	input = a0	output = sum2
4	5.32370e-10	input = a0	output = sum3
5	5.50721e-10	input = a1	output = sum0
6	5.14249e-10	input = a1	output = sum1
7	4.79123e-10	input = a1	output = sum2
8	5.32370e-10	input = a1	output = sum3
9	5.50721e-10	input = a2	output = sum0
10	5.14249e-10	input = a2	output = sum1
11	4.79123e-10	input = a2	output = sum2
12	5.32370e-10	input = a2	output = sum3
13	5.50721e-10	input = a3	output = sum0
14	5.14249e-10	input = a3	output = sum1
15	4.79123e-10	input = a3	output = sum2
16	5.32370e-10	input = a3	output = sum3
17	4.98113e-10	input = b0	output = sum0
18	4.99388e-10	input = b0	output = sum1
19	5.13420e-10	input = b0	output = sum2
20	4.99472e-10	input = b0	output = sum3
21	4.98113e-10	input = b1	output = sum0
22	4.99388e-10	input = b1	output = sum1
23	5.13420e-10	input = b1	output = sum2
24	4.99472e-10	input = b1	output = sum3
25	4.98113e-10	input = b2	output = sum0
26	4.99388e-10	input = b2	output = sum1
27	5.13420e-10	input = b2	output = sum2
28	4.99472e-10	input = b2	output = sum3
29	4.98113e-10	input = b3	output = sum0
30	4.99388e-10	input = b3	output = sum1
31	5.13420e-10	input = b3	output = sum2
32	4.99472e-10	input = b3	output = sum3
33			


Critical Path: input = a0 output = sum0  
Maximum Delay: 5.50721e-10

Subtractor:

```
≡ output_sub.txt
1  7.04016e-10 input = a0 output = sub0
2  6.91497e-10 input = a0 output = sub1
3  6.65262e-10 input = a0 output = sub2
4  6.27227e-10 input = a0 output = sub3
5  7.04016e-10 input = a1 output = sub0
6  6.91497e-10 input = a1 output = sub1
7  6.65262e-10 input = a1 output = sub2
8  6.27227e-10 input = a1 output = sub3
9  7.04016e-10 input = a2 output = sub0
10 6.91497e-10 input = a2 output = sub1
11 6.65262e-10 input = a2 output = sub2
12 6.27227e-10 input = a2 output = sub3
13 7.04016e-10 input = a3 output = sub0
14 6.91497e-10 input = a3 output = sub1
15 6.65262e-10 input = a3 output = sub2
16 6.27227e-10 input = a3 output = sub3
17 9.91639e-10 input = b0 output = sub0
18 9.13094e-10 input = b0 output = sub1
19 9.26857e-10 input = b0 output = sub2
20 8.74684e-10 input = b0 output = sub3
21 9.91639e-10 input = b1 output = sub0
22 9.13094e-10 input = b1 output = sub1
23 9.26857e-10 input = b1 output = sub2
24 8.74684e-10 input = b1 output = sub3
25 9.91639e-10 input = b2 output = sub0
26 9.13094e-10 input = b2 output = sub1
27 9.26857e-10 input = b2 output = sub2
28 8.74684e-10 input = b2 output = sub3
29 9.91639e-10 input = b3 output = sub0
30 9.13094e-10 input = b3 output = sub1
31 9.26857e-10 input = b3 output = sub2
32 8.74684e-10 input = b3 output = sub3
33
```

```
Critical Path: input = b0 output = sub1
Maximum Delay: 9.91639e-10
```

And Block:

Delay\_Analysis >  output\_and.txt

```
1    6.47381e-10 input = a0 output = and0
2    6.48628e-10 input = a0 output = and1
3    6.45373e-10 input = a0 output = and2
4    6.41169e-10 input = a0 output = and3
5    6.47381e-10 input = a1 output = and0
6    6.48628e-10 input = a1 output = and1
7    6.45373e-10 input = a1 output = and2
8    6.41169e-10 input = a1 output = and3
9    6.47381e-10 input = a2 output = and0
10   6.48628e-10 input = a2 output = and1
11   6.45373e-10 input = a2 output = and2
12   6.41169e-10 input = a2 output = and3
13   6.47381e-10 input = a3 output = and0
14   6.48628e-10 input = a3 output = and1
15   6.45373e-10 input = a3 output = and2
16   6.41169e-10 input = a3 output = and3
17   2.25989e-10 input = b0 output = and0
18   2.41673e-10 input = b0 output = and1
19   2.42316e-10 input = b0 output = and2
20   2.42261e-10 input = b0 output = and3
21   2.25989e-10 input = b1 output = and0
22   2.41673e-10 input = b1 output = and1
23   2.42316e-10 input = b1 output = and2
24   2.42261e-10 input = b1 output = and3
25   2.25989e-10 input = b2 output = and0
26   2.41673e-10 input = b2 output = and1
27   2.42316e-10 input = b2 output = and2
28   2.42261e-10 input = b2 output = and3
29   2.25989e-10 input = b3 output = and0
30   2.41673e-10 input = b3 output = and1
31   2.42316e-10 input = b3 output = and2
32   2.42261e-10 input = b3 output = and3
33
```

```
Critical Path: input = a0 output = and1
Maximum Delay: 6.48628e-10
```

Comparator:

Less than:

tpd	=	7.89336e-10	input = a0	output = l
tpd	=	7.89336e-10	input = a1	output = l
tpd	=	7.89336e-10	input = a2	output = l
tpd	=	7.89336e-10	input = a3	output = l
tpd	=	5.62867e-10	input = b0	output = l
tpd	=	5.62867e-10	input = b1	output = l
tpd	=	5.62867e-10	input = b2	output = l
tpd	=	5.62867e-10	input = b3	output = l

Critical Path: input = a0 output = l  
Maximum Delay: 7.89336e-10

Equal to:

tpd	=	3.03934e-09	input = a0	output = e
tpd	=	3.03934e-09	input = a1	output = e
tpd	=	3.03934e-09	input = a2	output = e
tpd	=	3.03934e-09	input = a3	output = e
tpd	=	9.05929e-10	input = b0	output = e
tpd	=	9.05929e-10	input = b1	output = e
tpd	=	9.05929e-10	input = b2	output = e
tpd	=	9.05929e-10	input = b3	output = e

Critical Path: input = a0 output = e  
Maximum Delay: 3.03934e-09



Greater than:

tpd	=	6.63572e-10	input = a0	output = g
tpd	=	6.63572e-10	input = a1	output = g
tpd	=	6.63572e-10	input = a2	output = g
tpd	=	6.63572e-10	input = a3	output = g
tpd	=	6.84783e-10	input = b0	output = g
tpd	=	6.84783e-10	input = b1	output = g
tpd	=	6.84783e-10	input = b2	output = g
tpd	=	6.84783e-10	input = b3	output = g


Critical Path: input = b0 output = g  
Maximum Delay: 6.84783e-10

ADDITIONAL: Stick diagrams for NOT, 2 input AND, OR, XOR, XNOR for implementation in MAGIC. All the circuits were a combination of these gates extrapolated to the required inputs

NOT

  


AND

 





XOR

 

OR

 

XNOR

 



### Further Optimization:

I could have combined the adder/subtractor blocks by taking the OR of D0 and D1 and sending that to a singular Enable block which would connect enabled B outputs to XOR with D1. The outputs of the latter and the enabled A outputs then can be sent to the 4 bit full adder. Also, for less than operation we need not remake the complex circuit and instead take XNOR of the greater than and equal to outputs. I could have also used a 3 input and gate for the AND block combining the enable and current and block.